
 


FPGA & Pulse Width Modulation

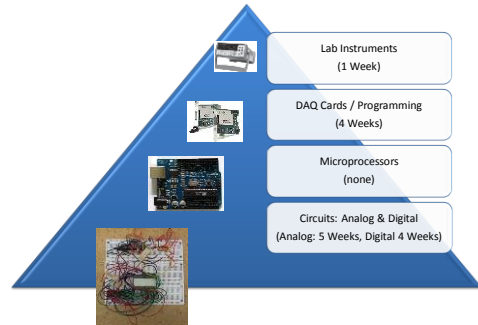


BFY
 BFY Workshop 30 University of Maryland 2015
 Kurt Wick (wick@umn.edu)
 University of Minnesota

Time Allotment During the First 14 Weeks of Our Advanced Lab Course



Digital Logic

 


- Rules of Digital logic are relatively few but (interesting) designs often require:
 - Large number of components
 - Fast clock speeds
- Conclusion: today's circuit very rarely use the old ASSP (Application-Specific Standard Products) such as the 74 series gates.
- They either use ASIC (Application Specific Integrated Circuits) or FPGAs or CPLDs.

Field Programmable Gate Arrays (FPGAs) and Complex Programmable Logic Devices (CPLDs)


- Number of Generic Gates: 100 000 to a few millions.
- Number of Flip-Flops: 2000 and above
- Clock Speed: 25 MHz up to GHz range.
- Pins: 100 to 400.
- Cost: a few dollars



Programming the FPGA

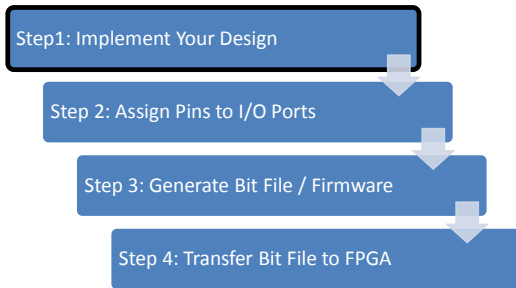


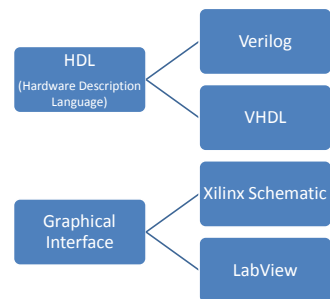Step 1: Implementing Your Design Approaches



Implementing Your Design in a Graphical Environment: Creating a 4 Bit Full Adder

Simple 1 Bit Adder

 


4-Bit Adder



Implementing Your Design in a Graphical Environment (continued)

 - Eas(ier) to learn than HDL
- **Displays parallel nature of circuits!**
- No Standard
- LabView Version will only work with LabView boards.



Step 1: Implementing Your Design in HDL

Verilog

- Users: 50%
- C-Based: Case sensitive
- [IEEE Standard 1364-2005](#)

```
module MyAndGate(
  input a,
  input b,
  output q);
  assign q = a&b;
endmodule
```

VHDL

- Users: 50%
- Based on ADA: not case sensitive
- [IEEE Standard 1076-2008](#)

```
-- import std_logic from the IEEE library
library IEEE;
use IEEE.std_logic_1164.all;


-- this is the entity
entity ANDGATE is
  port (
    I1 : in std_logic;
    I2 : in std_logic;
    O : out std_logic);
end entity ANDGATE;

-- this is the architecture
architecture RTL of ANDGATE is
  begin
    O <= I1 and I2;
end architecture RTL;
```

Student Lab Assignment: Radiation Counter




Block Diagram

 


PWM Theory
 
$$\langle V_{out} \rangle = \frac{\tau_{on}}{\tau_{swc}} V_{on}$$



PWM Circuit Components

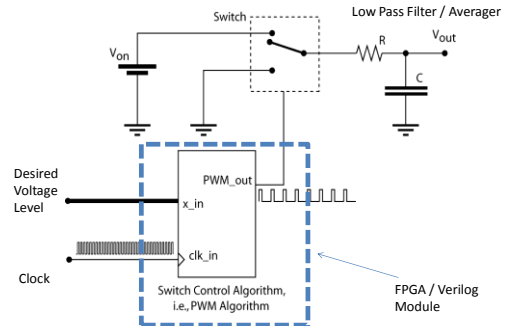


Simple PWM Control Algorithm

- An *n*-bit counter continuously increments from 0 to its maximum value, i.e., 2^n-1 and then repeats the cycle.
- Range of input value x_{in} : $0 \leq x_{in} \leq 2^n-1$

```

 if ( counter < x_in )
    PWM_out <= 1;
else
    PWM_out <= 0;
counter <= counter+1;
    
```




Verilog Implementation of Simple 8 Bit PWM Algorithm

```

module SimplePWM(clk_in, x_in, PWM_out);
    input clk_in; //clock for counter
    input [7:0] x_in; //control value that //defines pulse width //PWM signal out
    output reg PWM_out = 1;

    reg [7:0] counter = 0;

     always@ (posedge clk_in )begin
        if ( counter < x_in )
            PWM_out <= 1;
        else
            PWM_out <= 0;
        counter <= counter+1;
    end
endmodule
    
```



A2D Key Concepts: Resolution / Sensitivity

- Resolution of an *n*-bit PWM A2D is: $V_{on} / 2^n$
- (Hypothetical) Resolution for our BASYS board PWM A2D with $V_{on} = 5$ Volts would be:

bits	Resolution (Volts)
8	1.9E-02
16	7.6E-05
32	1.2E-09
64	2.7E-19


A2D Key Concepts: Conversion Time

- It takes at least one complete counter cycle to average V_{out} . For a counter running at f_o , this corresponds to: $2^n/f_o$
- (Optimal) Conversion Time for our BASYS board PWM A2D with $f_o = 25$ MHz:

Bits	Resolution (Volts)	Conversion Time
8	1.9E-02	10.2 usec
16	7.6E-05	2.6 msec
32	1.2E-09	2.8 min
64	2.7E-19	23000 years

Sigma Delta Concepts

 
Though $V_{out}(t)$ is different in each of these timing diagrams, $\langle V_{out} \rangle$ remains identical.




Sigma Delta PWM Algorithm

```

 if ( Sigma >= Delta )
{
    Sigma = (Sigma - Delta) + x_in;
    Out = 1;
}
else
{
    Sigma = Sigma + x_in;
    Out = 0;
}
    
```



PWM Application: Music Player

 


Conclusions about PWM

- Pulse Width Modulation can be used to create an analog signal from a digital signal.
- Allows the reduction of a DC signal while being much more energy efficient than, for example, a passive voltage divider.
- Sigma Delta algorithm can also be used for voltage to frequency conversion.

Educational Goals


- The PWM exercises expose students to basic digital concepts such as clocks and counters.
- They are easily implemented with an FPGA and thereby exposes students with this ubiquitous electronic component.
- Familiarizes them with digital-to-analog converters and the basic concepts of resolution and conversion time.
- The exercise can be extended by turning it into an analog-to-digital converter using successive approximation and a state machine.

Successive Approximation A2D

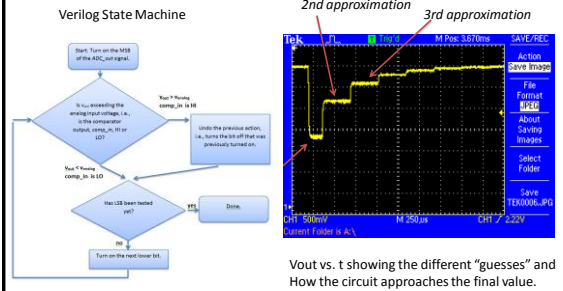


Successive Approximation A2D

Verilog State Machine

 

IP (Intellectual Property) Cores


 
- Add New Source: in the Source Wizard select: IP (CORE Generator and Architecture Wizard.)
- Free IP Cores in the ISE Webpack:
 - Signal Processing: FIR Filters
 - Transforms: FFT
 - Math Functions (Trig, Divide, Square Root etc.)
 - Embedded Microprocessors



- Using a Trigonometric IP Core to Create an Arbitrary Waveform

Additional Projects: Using IP Cores for Embedded Designs

  Using a Microprocessor to Communicate with the PC



Additional Resources

- Books
 - Advanced Digital Design with the Verilog HDL (2nd Edition) [Hardcover] Michael D. Ciletti
- Web Sites
 - Opencores is a website that lets users upload and download their VHDL and Verilog code. It contains a large repository for communications controllers (SPI, Serial etc) and microprocessors:
<http://opencores.org/>
 - Our Wiki Page:
<https://wiki.umn.edu/MXP/AlphaWorkshop>